

MEASUREMENT DEVICES

- Types Of Error
 1. Gross Error
 2. Systematic Error
 3. Random Error
 4. Absolute Error
 5. Relative Error
- Absolute Error

$$e = |Y_n - X_n|$$

e = Absolute Error

Y_n = Expected Value

X_n = Measured Value

- Relative Error

$$\text{Relative Error} = \frac{\text{Absolute}}{\text{Expected Value}}$$

$$\text{Relative Error} = \left| \frac{Y_n - X_n}{Y_n} \right|$$

$$\text{Relative Error} = \left| \frac{e}{Y_n} \right|$$

- Standard Used In Measurement
 - a. International Standards
 - b. The Primary Standards
 - c. Secondary Standards
 - d. Working Standards

- Principle Operation Of PMMC

1. Deflecting System
2. Controlling System
3. Damping System

- Deflecting Torque Equation

$$T_d = BAN I$$

T_d = deflecting Torque (Nm)

B = flux density in air gap (Wb/m^2) / T

N = number of turns of the coil

A = effective coil area ($w \times l$) (m^2)

I = Current in the moving coil (A)


- Single Range DC Ammeter
- Voltage Equation

$$R_{SH} = \frac{I_m R_m}{I_{SH}}$$

- Current Equation

$$R_{SH} = \frac{I_m R_m}{I - I_m}$$


- Two Range DC Ammeter

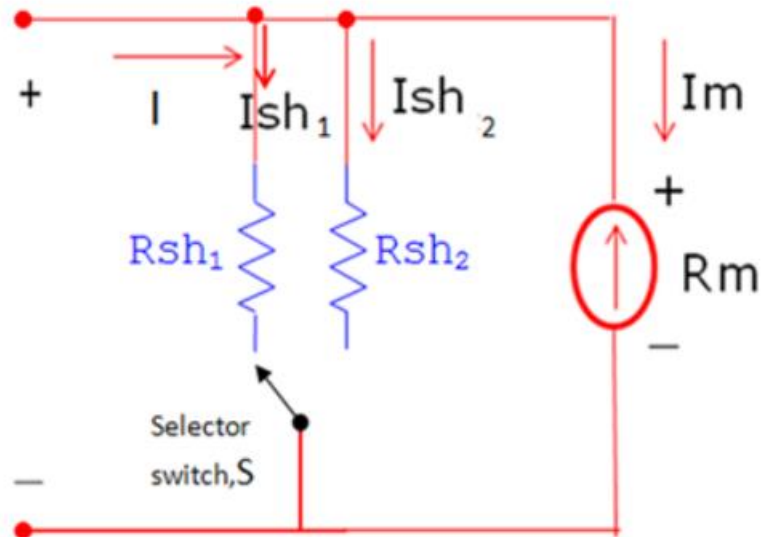

$V_m = \text{voltage drop across the } R_m \text{ IS EQUAL}$

$V_{sh1} = \text{voltage drop across the } R_{sh1}$

$$R_{sh1} = I_m R_m / I_1 - I_m$$

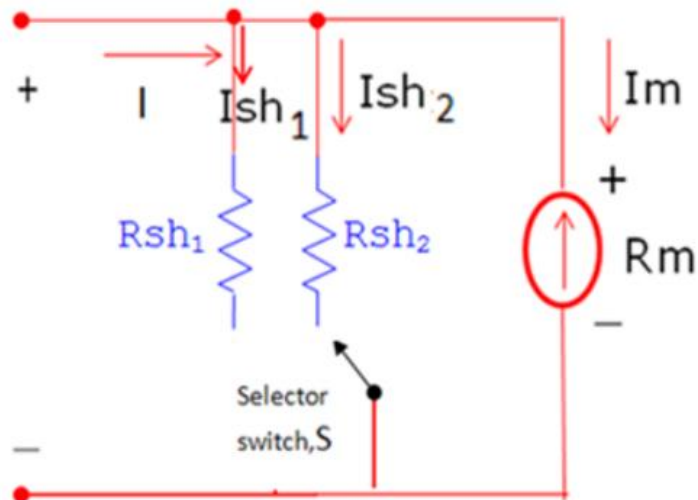


$V_m = \text{voltage drop across the } R_m \text{ IS EQUAL}$

$V_{sh2} = \text{voltage drop across the } R_{sh2}$

$$R_{sh2} = I_m R_m / I_2 - I_m$$

- Two Range DC Ammeters (Ayrton Shunt)

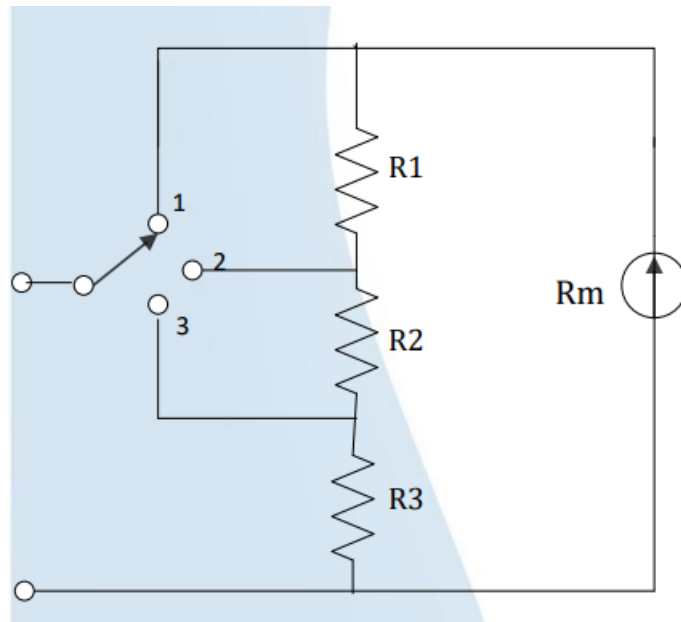

- If the input connect to position 1,

$$(I - I_m)(R_1 + R_2 + R_3) = I_m R_m$$

- If the input connect to position 2,

$$(I - I_m)(R_2 + R_3) = I_m(R_m + R_1)$$

- If the input connect to position 3,

$$(I - I_m)(R_3) = I_m(R_m + R_1 + R_2)$$

- Voltage Kirchoff Law

$$R_s = \frac{V}{I_m} - R_m$$


- Resistance Load

$$R_L = \frac{V}{I}$$

- Sensitivity Voltmeter

$$R_m = S \times V$$

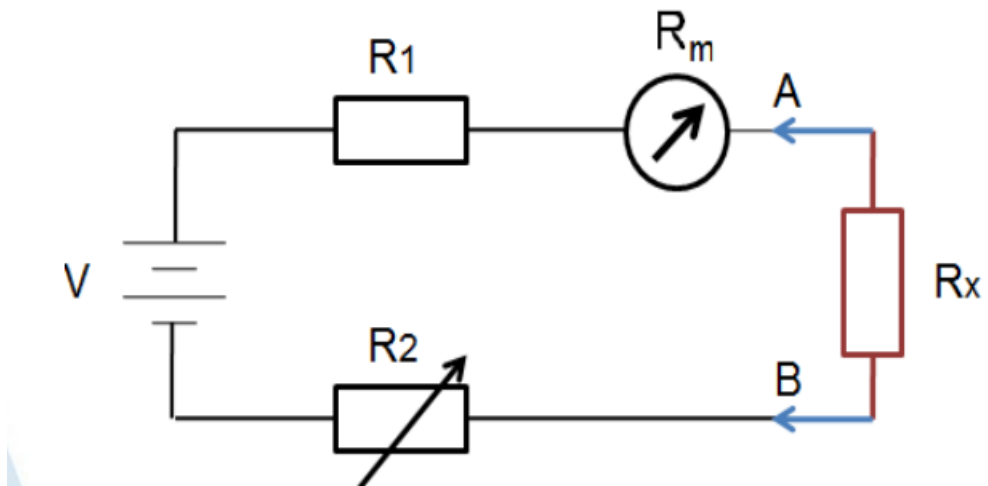
- Derivation Equation For Series Ohmmeter



$$R_T = R_m + R_1 + R_2 + R_x$$

$$R_x = R_T - R_m - R_1 - R_2$$

- Derivation Equation For Shunt Ohmmeter

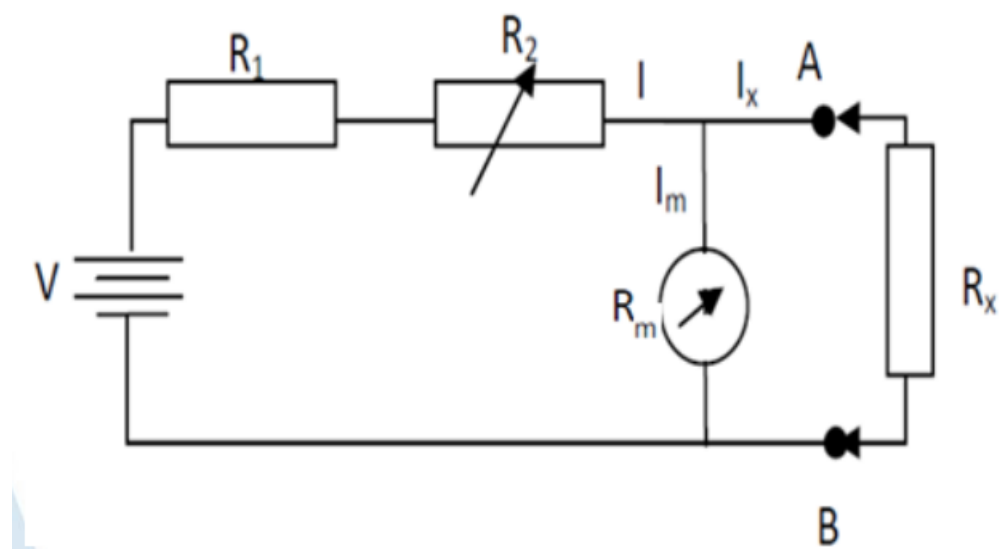

$$V_{KL} \dots V_m = V_x$$


$$V_x = I_x R_x$$

$$V_m = I_m R_m$$

$$CKL \dots \frac{I_m R_m}{I_x}$$

$$I_x = I - I_m$$

- AC Measurement

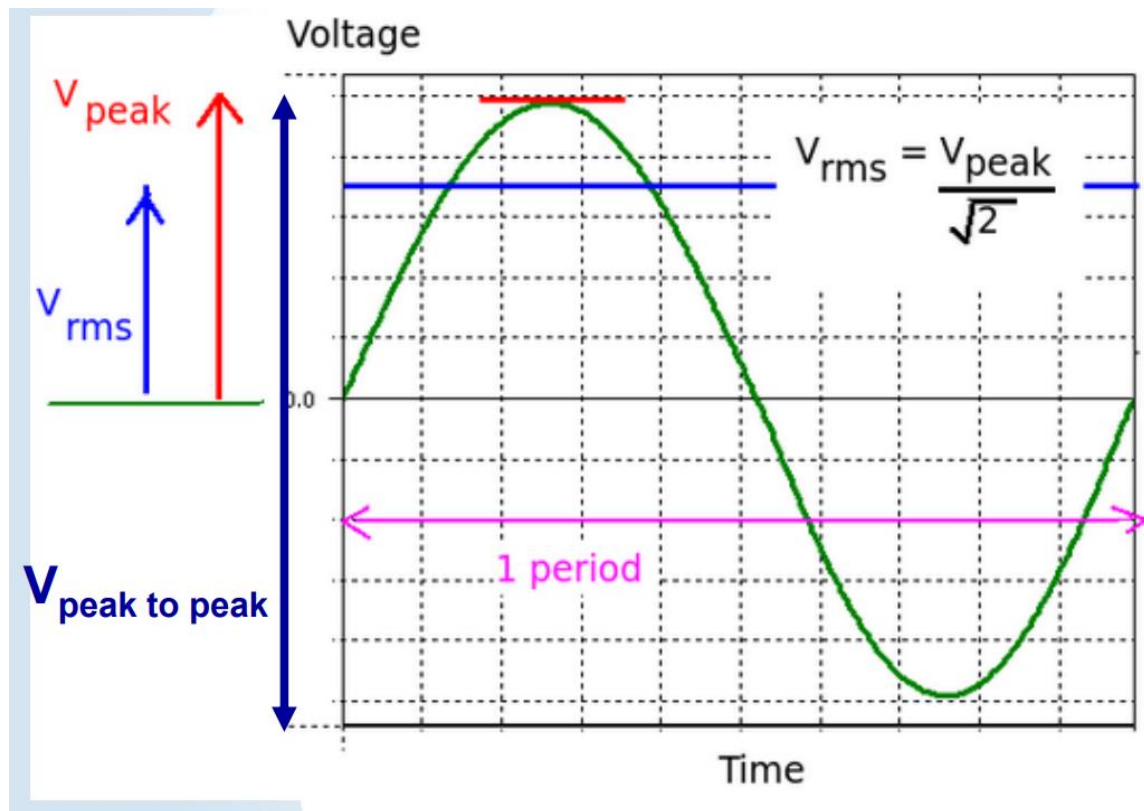

- Voltage Peak, V_p

$$\text{No. of Div}_{(\text{peak})} \times (\text{volt/div})$$

- Voltage Peak to Peak, V_{pp}

$$\text{No. of Div}_{(\text{peak to peak})} \times (\text{volt/div})$$

- Voltage Root Mean Square, V_{rms}

$$\frac{V_p}{\sqrt{2}} = 0.707V_p$$

- Frequency

$$f = \frac{1}{T}$$

(Unit : Hz)

- Time

$$\text{No. of Division} \times \left(\text{time} / \text{div} \right)$$

(Unit : s)

- Phase Measurement

$$\theta = \frac{\Delta t}{T} \times 360^\circ$$

- Phase Different in XY Mode (Lissajous figure)

$$\text{Phase Angle, } \theta = \sin^{-1} \left(\frac{A}{B} \right)$$

A = peak to peak vertical height of the ellipse

B = is the intercept on the Y-axis

- Power

$$P = IV, \quad P = I^2 R, \quad P = \frac{V^2}{R}$$

- Energy

$$\text{Power} \times \text{time}(\text{joules})$$